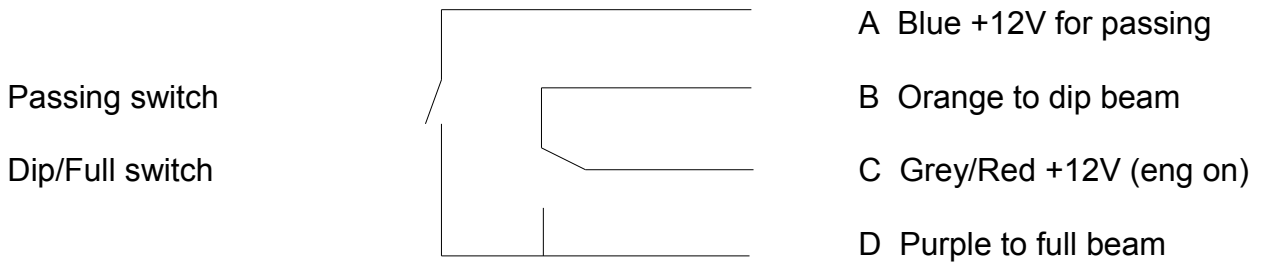



Dipped lamp always on mod for Fuoco/MP3 500
 (colours may not apply to other models, switch positions do)

I thought I'd try to investigate the headlamp switching. The switch is actually two switches:



The Grey/Red wire is fed from an engine-on relay, and the Blue is merely ignition controlled.

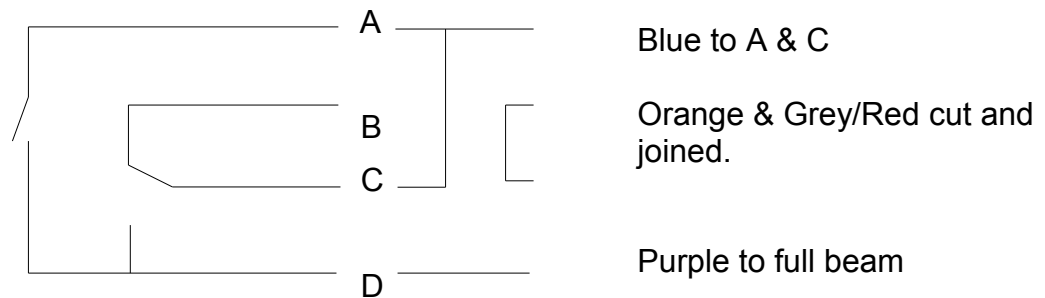The wires to B and C can be cut, joined and insulated, and the feed to A also paralleled to C. This ensures the dipped beam is always on when the engine is running, and the switch merely turns on the full beam either latched or momentarily.



This is what I've done, and it works well.